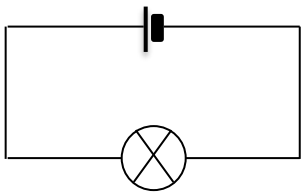
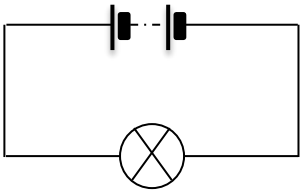
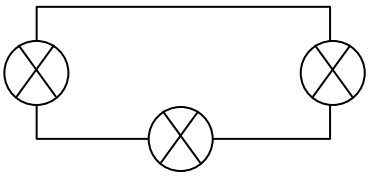
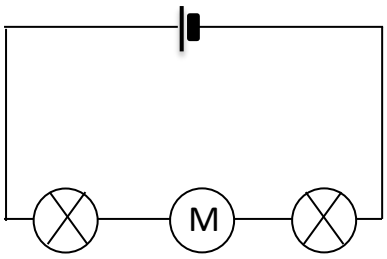
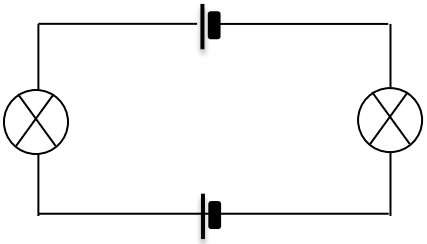
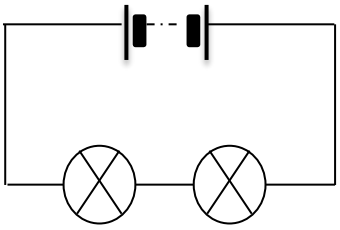
Circuits Name.....

Circuit 1	Circuit 2	Circuit 3
		
Will this circuit work?	Will this circuit work?	Will this circuit work?
Did it work when tested?	Did it work when tested?	Did it work when tested?
Notes	Notes	Notes
Circuit 4	Circuit 5	Circuit 6
		
Will this circuit work?	Will this circuit work?	Will this circuit work?
Did it work when tested?	Did it work when tested?	Did it work when tested?
Notes	Notes	Notes

©Mary Le Breuilly